

# Feedback and Oscillator Circuits

# Practical Feedback Circuits

## Voltage Series Feedback:


- A part of the output signal ( $V_o$ ) is obtained using a feedback network of resistors  $R_1$  and  $R_2$
- The feedback voltage  $V_f$  is connected in series with the source signal  $V_s$ , their difference being the input signal  $V_i$

$$V_f = \frac{R_1}{R_1 + R_2} V_o$$

$$\beta = \frac{V_f}{V_o} = \frac{R_1}{R_1 + R_2}$$

$$A_f = \frac{A}{1 + A\beta} = \frac{\infty}{1 + \frac{R_1}{R_1 + R_2} \cdot \infty} \approx \frac{\infty}{\infty \cdot \frac{R_1}{R_1 + R_2}}$$
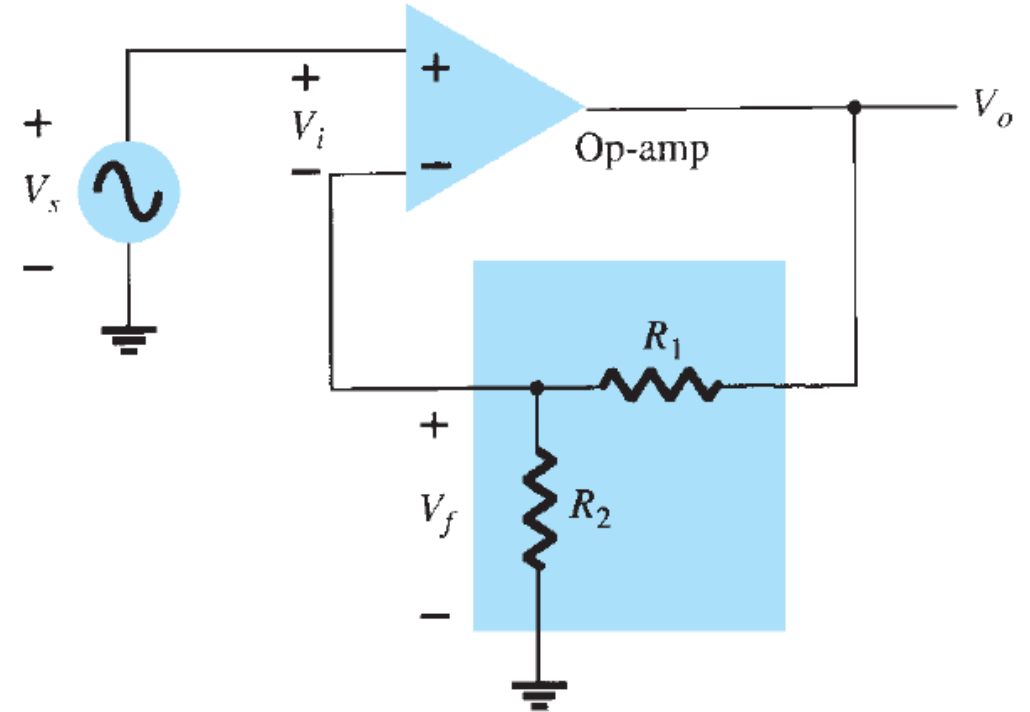
$$A_f = \frac{R_1 + R_2}{R_1} = 1 + \frac{R_2}{R_1}$$



# Practical Feedback Circuits

## Voltage Series Feedback:

Without feedback the amplifier gain is

$$A = \frac{V_o}{V_i} = -g_m R_L, \quad g_m = \frac{I_D}{V_{GS}}$$

where  $R_L$  is the parallel combination of resistors:

$$R_L = R_D // R_o$$


With feedback

$$\beta = \frac{V_f}{V_o} = \frac{-R_2}{R_1 + R_2}$$

$$A_f = \frac{A}{1 + \beta A} = \frac{-g_m R_L}{1 + [R_2 R_L / (R_1 + R_2)] g_m}$$

If  $\beta A \gg 1$ , we have
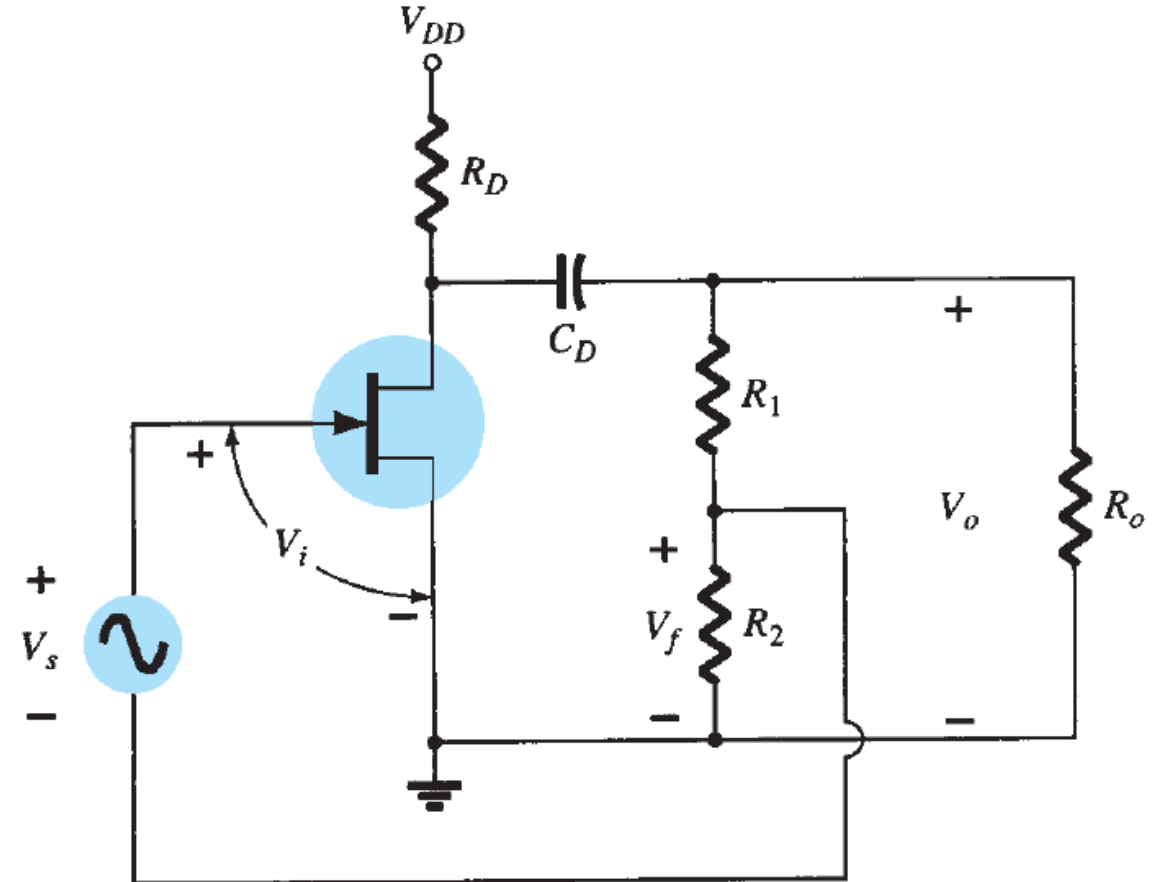
$$A_f \approx \frac{1}{\beta} = -\frac{R_1 + R_2}{R_2}$$



# Practical Feedback Circuits


## Voltage Series Feedback:

- The emitter-follower circuit provides voltage-series feedback
- The signal voltage  $V_s$  is the input voltage  $V_i$
- The output voltage  $V_o$  is also the feedback voltage in series with the input voltage
- The operation of the circuit without feedback provides  $V_f = 0$ , so that

$$A = \frac{V_o}{V_i} = \frac{(\beta_{tr} I_b) R_E}{V_i} = \frac{(\beta_{tr} I_b) R_E}{I_b (\beta_{tr} r_e)} = \frac{R_E}{r_e}$$

With feedback
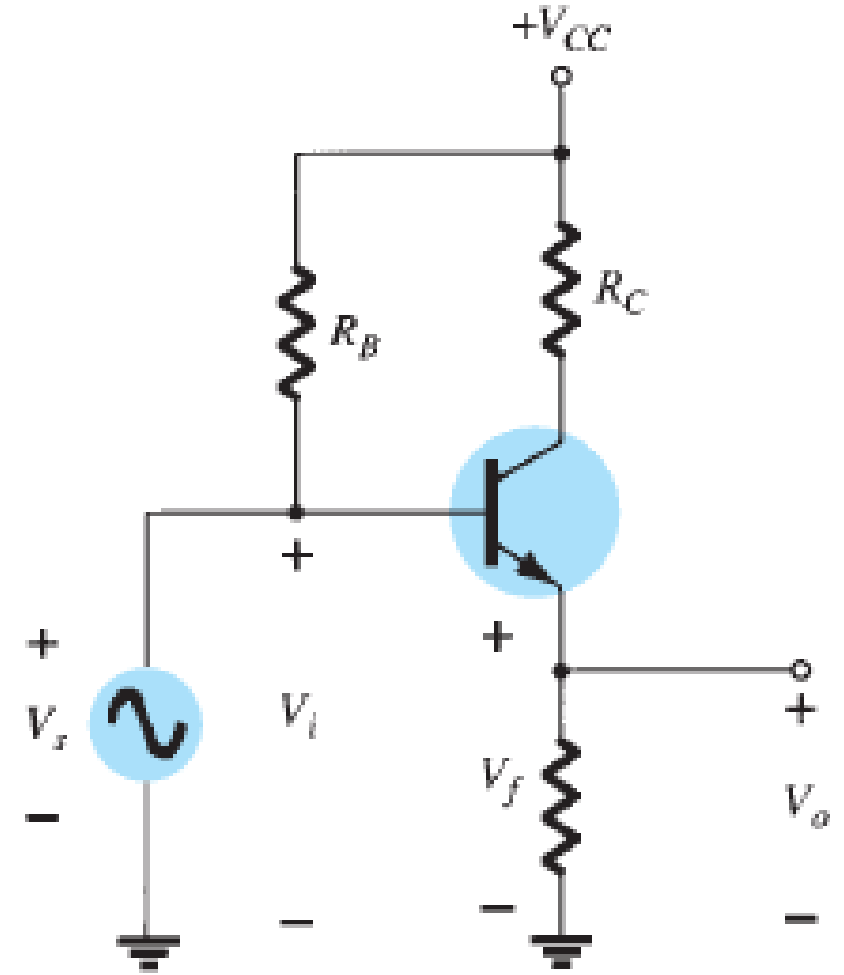
$$\begin{aligned} \beta &= \frac{V_f}{V_o} = 1 \\ A_f &= \frac{V_o}{V_s} = \frac{A}{1 + \beta A} = \frac{R_E / r_e}{1 + (1)(R_E / r_e)} \\ &= \frac{R_E}{r_e + R_E} \end{aligned}$$



# Practical Feedback Circuits

## Voltage Shunt Feedback:



Without feedback

$$A = \frac{V_o}{I_i} = \frac{V_o}{0} = \infty$$

$$\beta = \frac{I_f}{V_o} = \frac{-1}{R_o}$$

With feedback

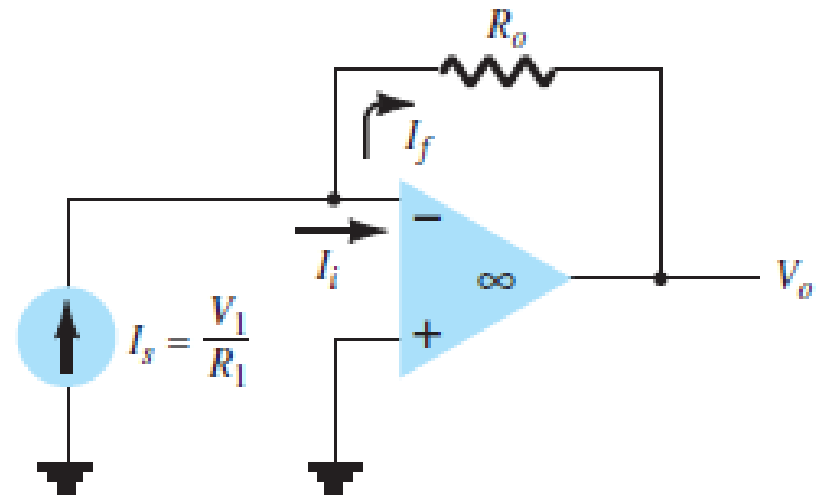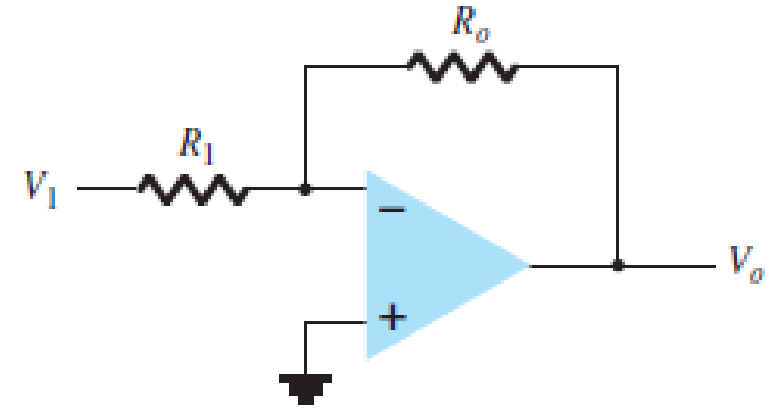
$$A_f = \frac{V_o}{I_s} = \frac{A}{1 + \beta A} \approx \frac{1}{\beta} = -R_o$$


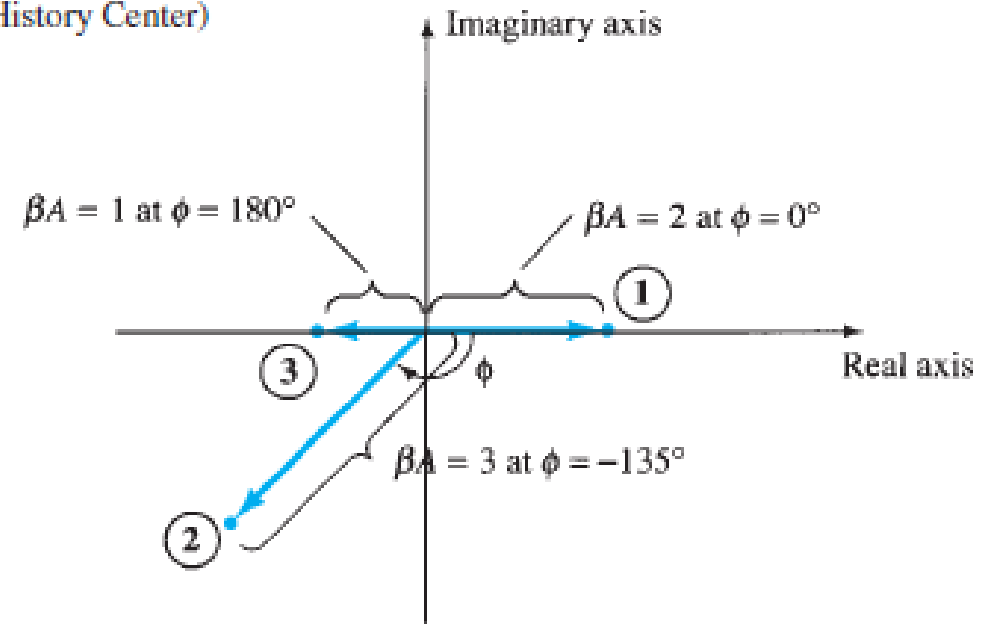
# Phase and Frequency Considerations

- Stability of a feedback amplifier is determined by the  $\beta A$  product and the phase shift between input and output
- One of the most popular techniques used to investigate stability is the Nyquist method
- A Nyquist diagram is used to plot gain and phase shift as a function of frequency on a complex plane
- The Nyquist plot, in effect, combines the two Bode plots of gain versus frequency and phase shift versus frequency on a single plot
- A Nyquist plot is used to quickly show whether an amplifier is stable for all frequencies and how stable the amplifier is relative to some gain or phase-shift criteria
- As a start, consider the *complex plane* shown in figure
- A few points of various gain ( $\beta A$ ) values are shown at a few different phase-shift angles


(Courtesy of AT&T Archives and History Center)


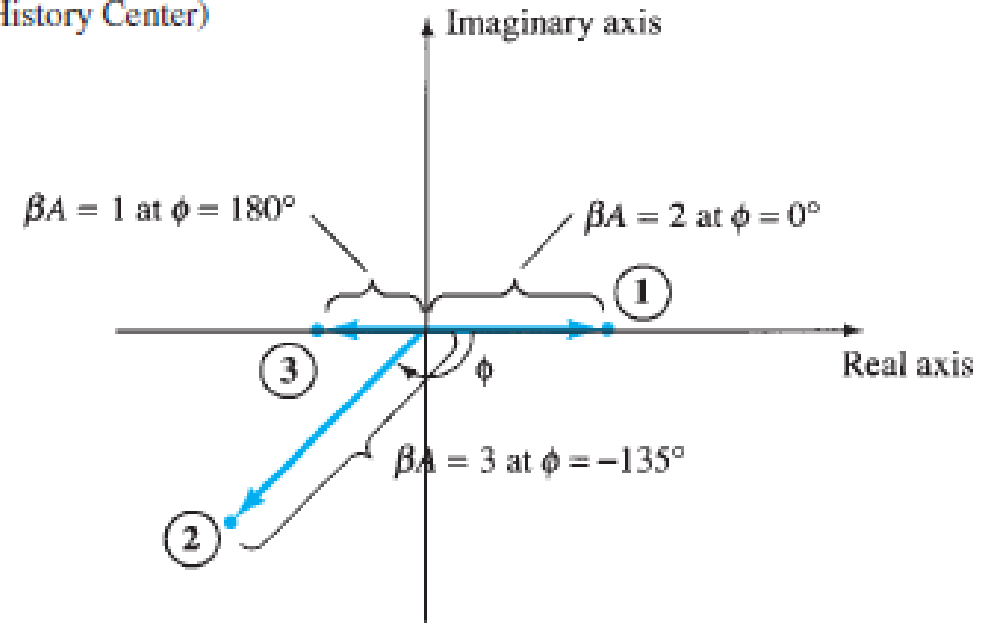
# Phase and Frequency Considerations

- As a start, consider the *complex plane* shown in figure
- A few points of various gain ( $\beta A$ ) values are shown at a few different phase-shift angles
- By using the positive real axis as reference ( $0^\circ$ ), we see a magnitude of  $\beta A = 2$  at a phase shift of  $0^\circ$  at point 1
- Additionally, a magnitude of  $\beta A = 3$  at a phase shift of  $135^\circ$  is shown at point 2
- And magnitude/phase of  $\beta A = 1$  at  $180^\circ$  is shown at point 3
- Thus points on this plot can represent *both* gain magnitude of  $\beta A$  and phase shift


(Courtesy of AT&T Archives and History Center)



# Phase and Frequency Considerations

- If the points representing gain and phase shift for an amplifier circuit are plotted at increasing frequency, then a Nyquist plot is obtained as shown by the plot
- At the origin, the gain is 0 at a frequency of 0 (for RC-type coupling)
- At increasing frequency, points  $f_1$ ,  $f_2$ , and  $f_3$  and the phase shift increase, as does the magnitude of  $\beta A$
- At a representative frequency  $f_4$ , the value of  $\beta A$  is the vector length from the origin to point  $f_4$  and the phase shift is the angle  $\phi$
- At a frequency  $f_5$ , the phase shift is  $180^\circ$
- At higher frequencies, the gain is shown to decrease back to 0
- The Nyquist criterion for stability can be stated as follows:


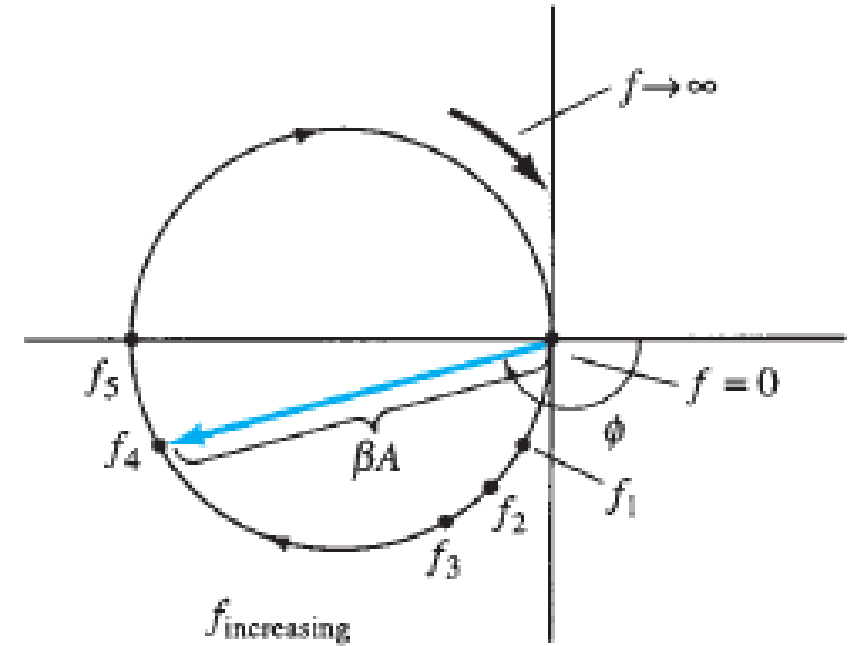
***The amplifier is unstable if the Nyquist curve encloses (encircles) the  $-1$  point, and it is stable otherwise.***





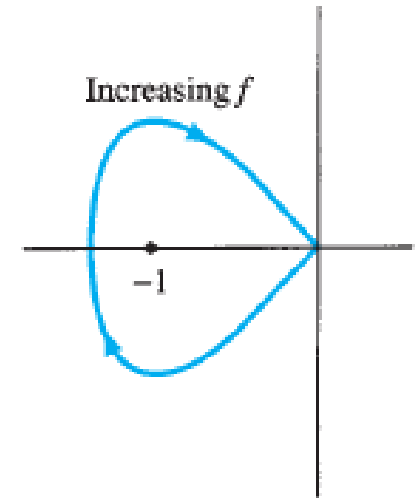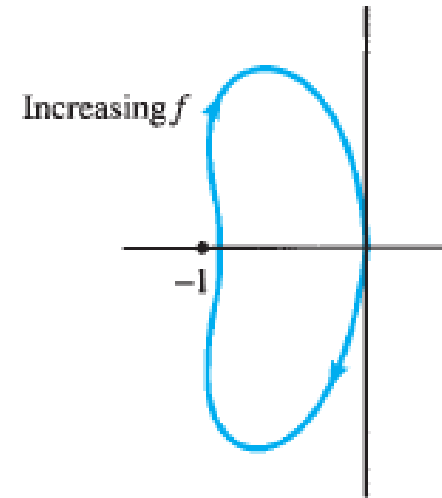
# Phase and Frequency Considerations

- An example of the Nyquist criterion is demonstrated by the curves in figures
- The Nyquist plot in figure on the left is stable since it does not encircle the 1 point
- Whereas the plot shown in figure on the right is unstable since the curve does encircle the -1 point
- Keep in mind that encircling the -1 point means that at a phase shift of  $180^\circ$  the loop gain ( $\beta A$ ) is greater than 1
- Therefore, the feedback signal is large enough to result in a larger input signal than that applied, with the result that oscillation occurs





# Phase and Frequency Considerations

- From the Nyquist criterion, we know that a feedback amplifier is stable if the loop gain ( $\beta A$ ) is less than unity (0 dB) when its phase angle is  $180^\circ$
- We can additionally determine some margins of stability to indicate how close to instability the amplifier is
- **Gain margin (GM)** is defined as the value of  $|\beta A|$  in decibels at the frequency at which the phase angle is  $180^\circ$
- Thus, 0 dB, equal to a value of  $\beta A=1$ , is on the border of stability and any negative decibel value is stable
- The GM may be evaluated in decibels from the curve of figure on top
- **Phase margin (PM)** is defined as  $180^\circ$  minus the absolute value of the angle at which the value  $|\beta A|$  is unity (0 dB)
- The PM may be evaluated directly from the curve of bottom figure

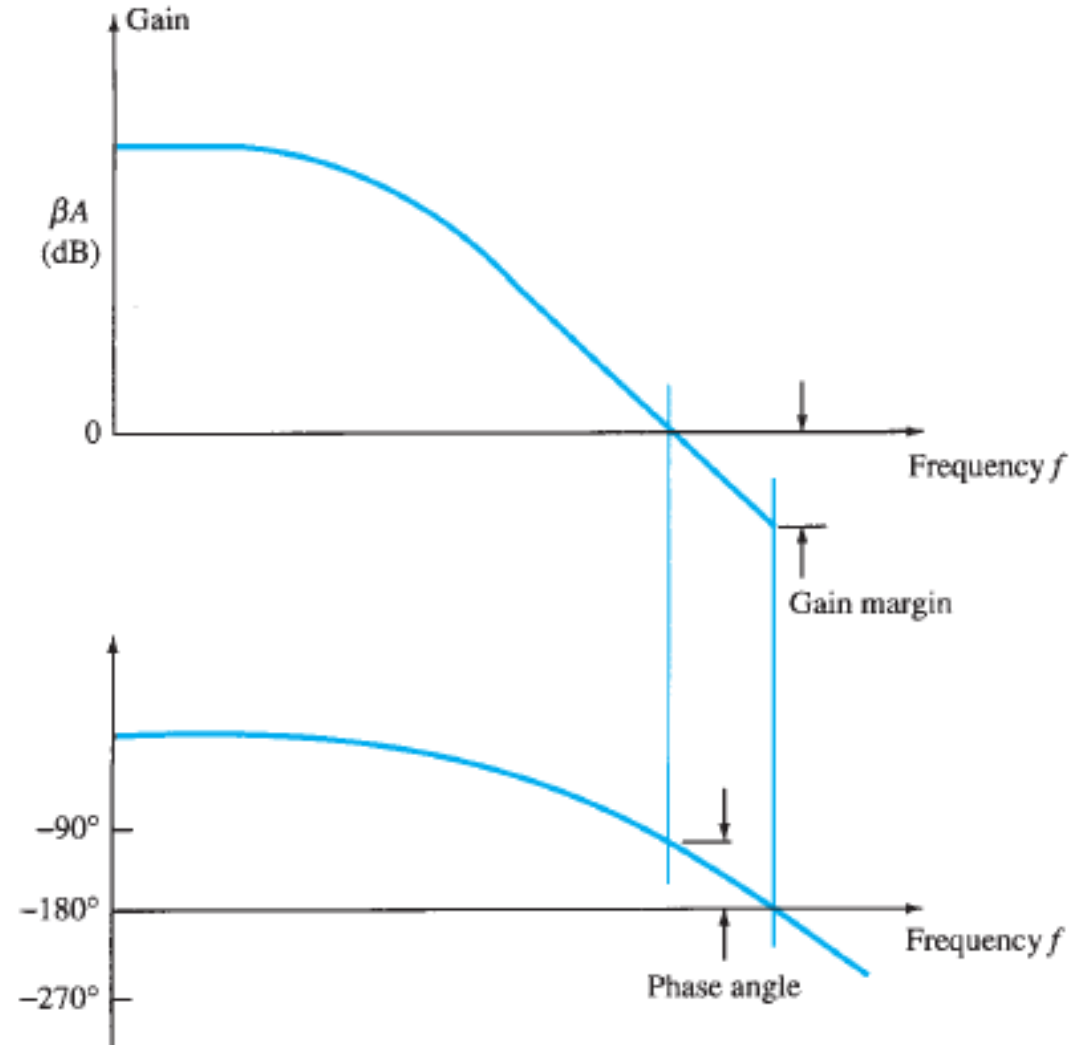


# Oscillators

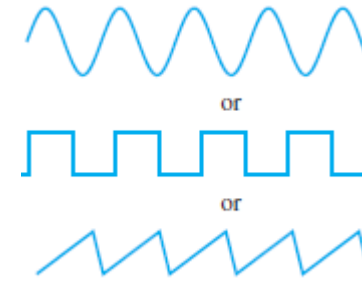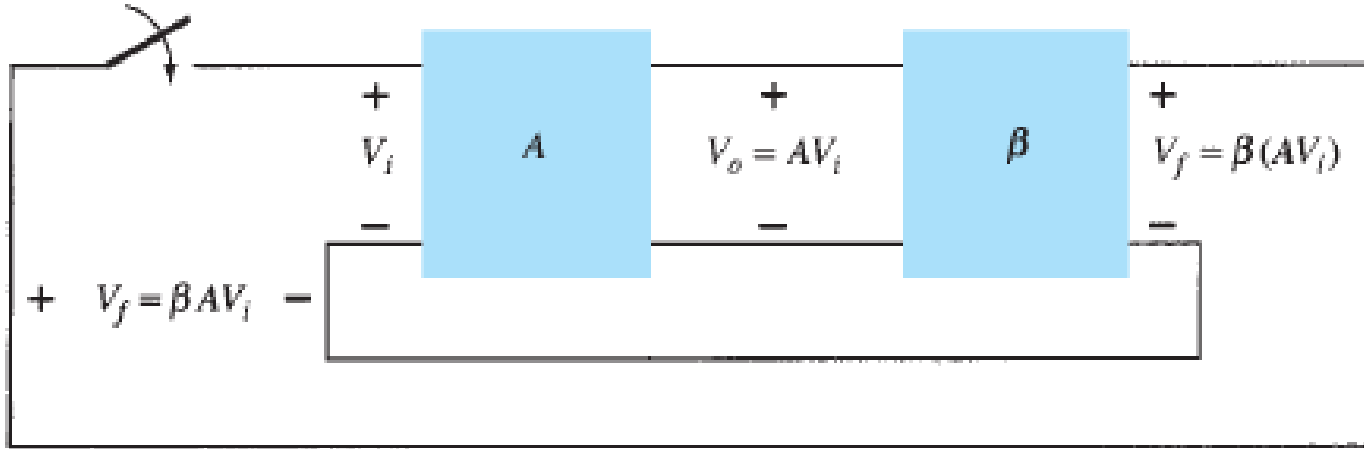

- The use of positive feedback that results in a feedback amplifier having closed-loop gain  $|\beta A|$  greater than 1 and satisfies the phase conditions will result in operation as an oscillator circuit
- An oscillator circuit then provides a varying output signal
- Consider the feedback circuit given in the figure
- When the switch at the amplifier input is open, no oscillation occurs


# Oscillators

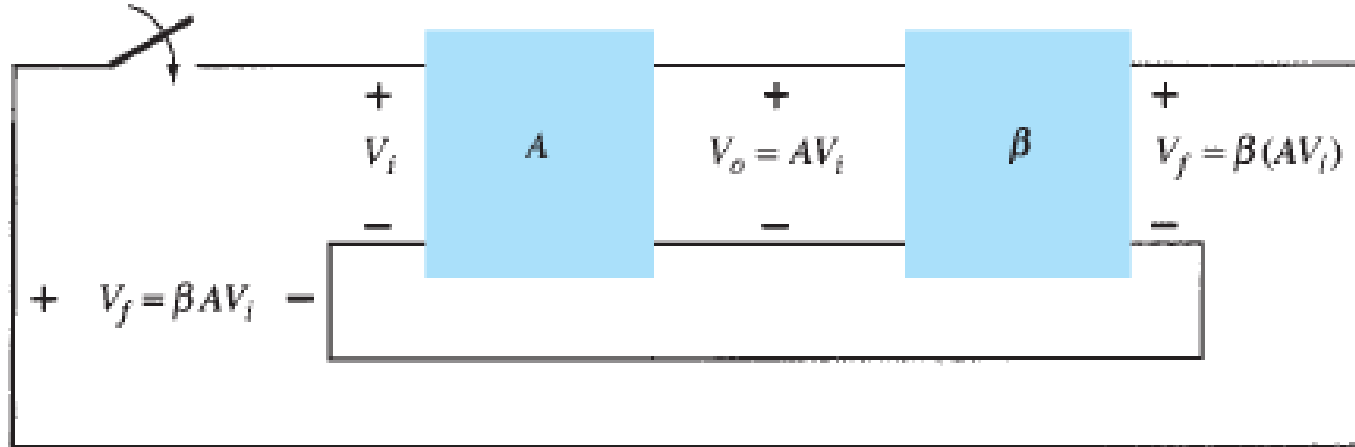

- Consider that we have a *fictitious* voltage at the amplifier input  $V_i$
- Results in output voltage  $V_o = AV_i$  and in feedback voltage  $V_f = \beta(AV_i)$
- If the circuits of the base amplifier and feedback network provide  $\beta A$  of a correct magnitude and phase,  $V_f$  can be made equal to  $V_i$
- Then, when the switch is closed and the fictitious voltage  $V_i$  is removed, the circuit will continue operating since the feedback voltage is sufficient to drive the circuit
- The output waveform will still exist after the switch is closed if the condition  $\beta A=1$  is met
- This is known as the *Barkhausen criterion* for oscillation.
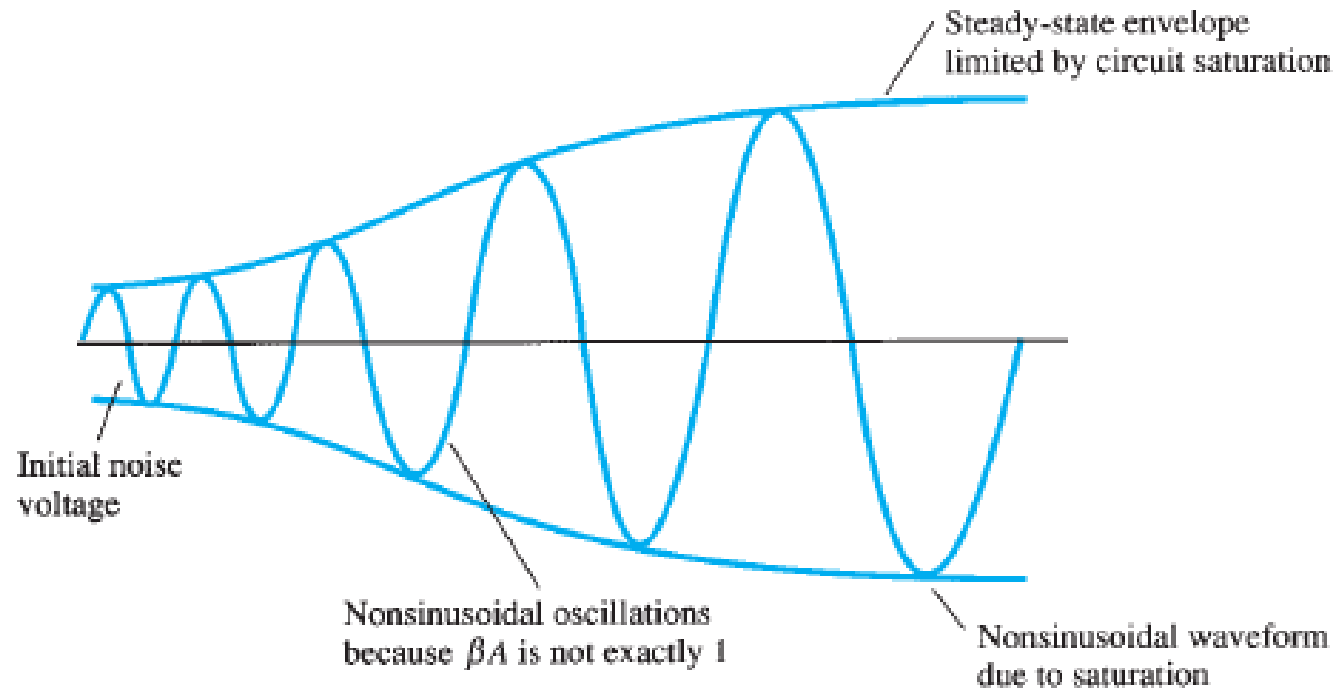
# Oscillators

- In reality, no input signal is needed to start the oscillator going
- Only the condition  $\beta A=1$  must be satisfied for self-sustained oscillations to result
- In practice,  $\beta A$  is made greater than 1, system starts oscillating by amplifying noise voltage, which is always present
- Saturation factors in the practical circuit provide an “average” value of  $\beta A$  of 1
- The resulting waveforms are never exactly sinusoidal
- However, the closer the value  $\beta A$  is to exactly 1, the more nearly sinusoidal is the waveform
- Figure below shows how the noise signal results in a buildup of a steady-state oscillation condition.




# Phase-Shift Oscillators

An idealized version of this circuit is shown in the figure.

We consider the feedback network to be driven by a perfect source (zero source impedance)

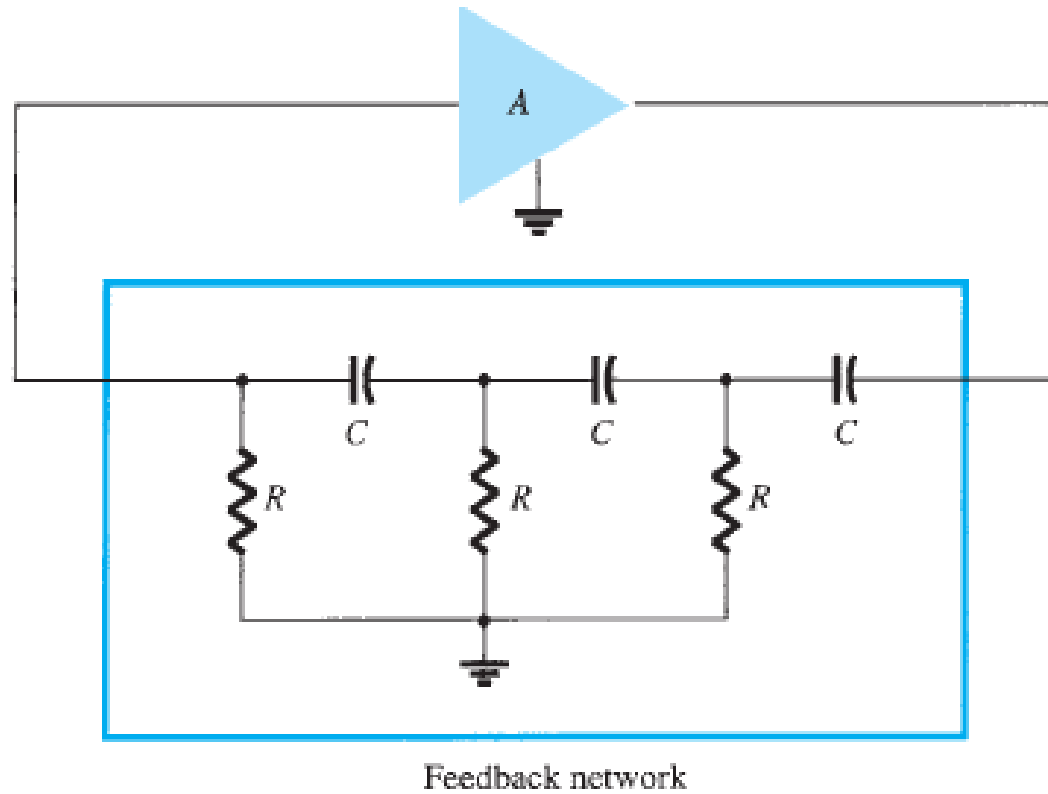And the output of the feedback network to be connected into a perfect load (infinite load impedance)





# Phase-Shift Oscillators

- An ideal single-pole RC circuit would produce a phase shift of exactly  $90^\circ$ , and because  $180^\circ$  of phase shift is required for oscillation, at least two single-poles must be used in an RC oscillator design
- However in reality it is difficult to obtain exactly  $90^\circ$  of phase shift so more stages are used
- The amount of actual phase shift is given as:



$$X_C = \frac{1}{2\pi fC} \Rightarrow Z = \sqrt{R^2 + X_C^2} \quad \& \quad \phi = \tan^{-1} \frac{X_C}{R}$$
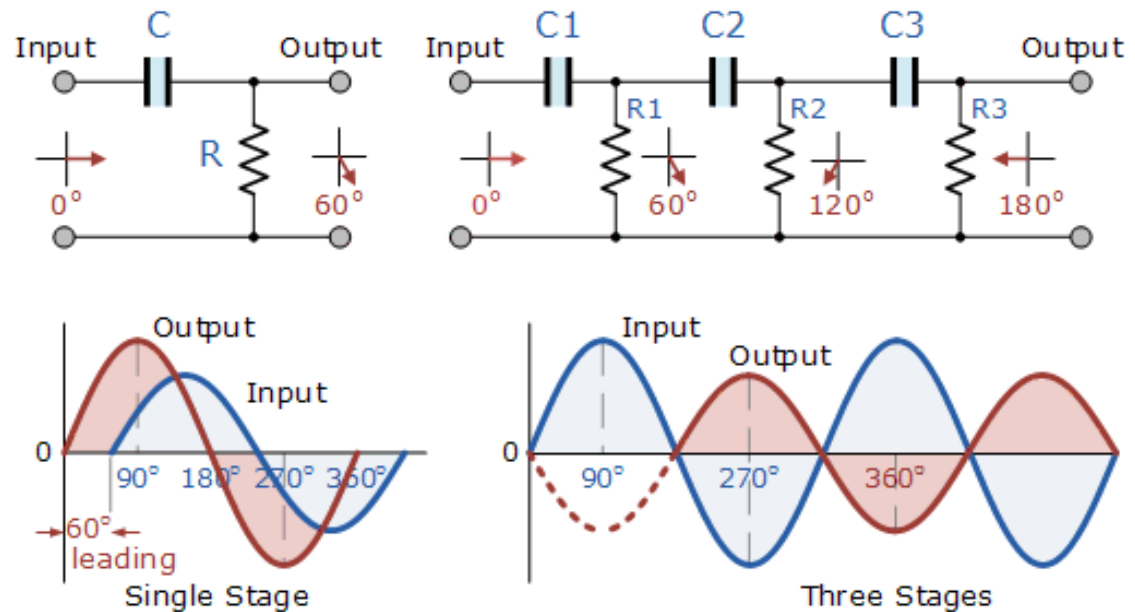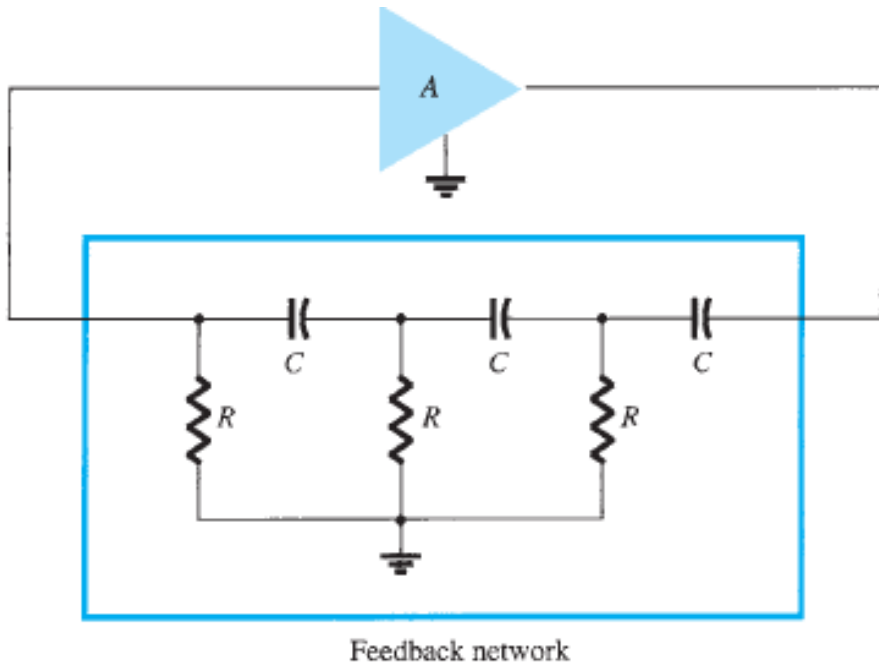
$$\text{for } \phi = 60^\circ, \tan^{-1} \frac{1}{2\pi fRC} = 60^\circ \Rightarrow \tan(60^\circ) = \sqrt{3} = \frac{1}{2\pi fRC} \Rightarrow f = \frac{1}{2\pi\sqrt{3}RC}$$


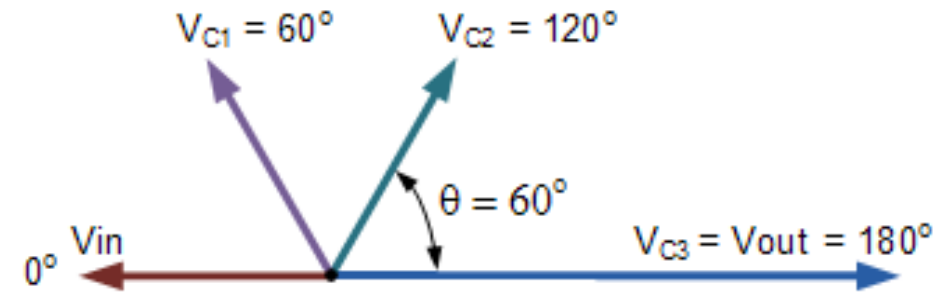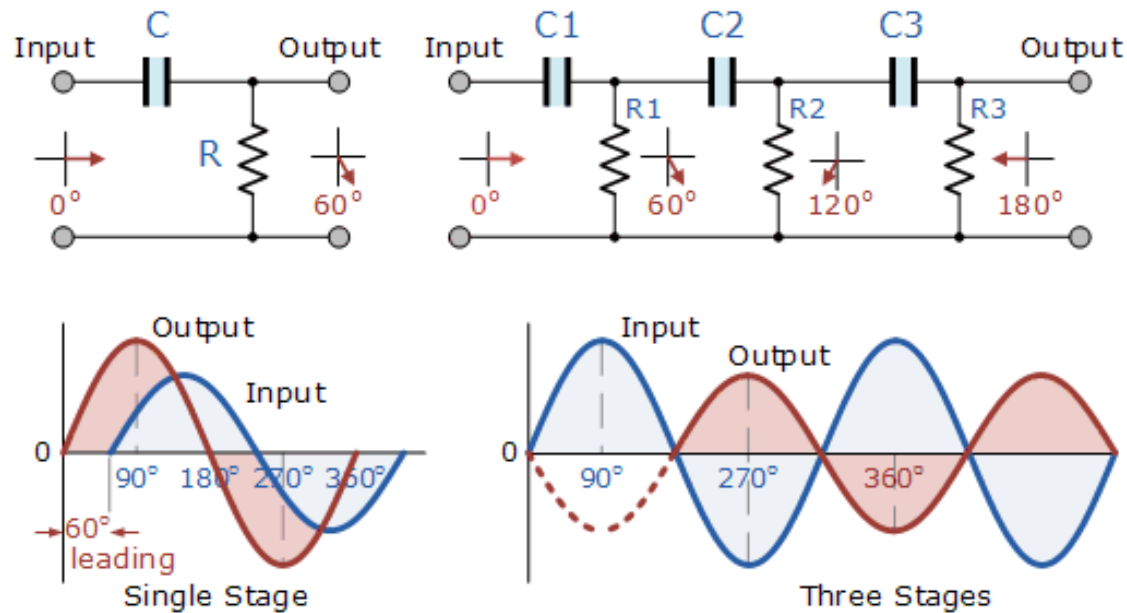
# Phase-Shift Oscillators

- Values of R and C have been chosen so that at the required frequency the output voltage leads the input voltage by an angle of about 60°
- Then the phase angle between each successive RC section increases by another 60° giving a phase difference between the input and output of 180° (3 x 60°) as shown by the following vector diagram\*
- If all the resistors, R and the capacitors, C in the phase shift network are equal in value, then the frequency of oscillations produced by the RC oscillator is given as:  $f = \frac{1}{2\pi RC\sqrt{6}}$  and  $\beta = \frac{1}{29}$



\* [http://www.electronics-tutorials.ws/oscillator/rc\\_oscillator.html](http://www.electronics-tutorials.ws/oscillator/rc_oscillator.html)




# FET Phase-Shift Oscillator


The amplifier stage is self-biased with a capacitor bypassed source resistor  $R_S$  and a drain bias resistor  $R_D$

$$A = -g_m R_D$$

$$f = \frac{1}{2\pi RC\sqrt{6}}$$

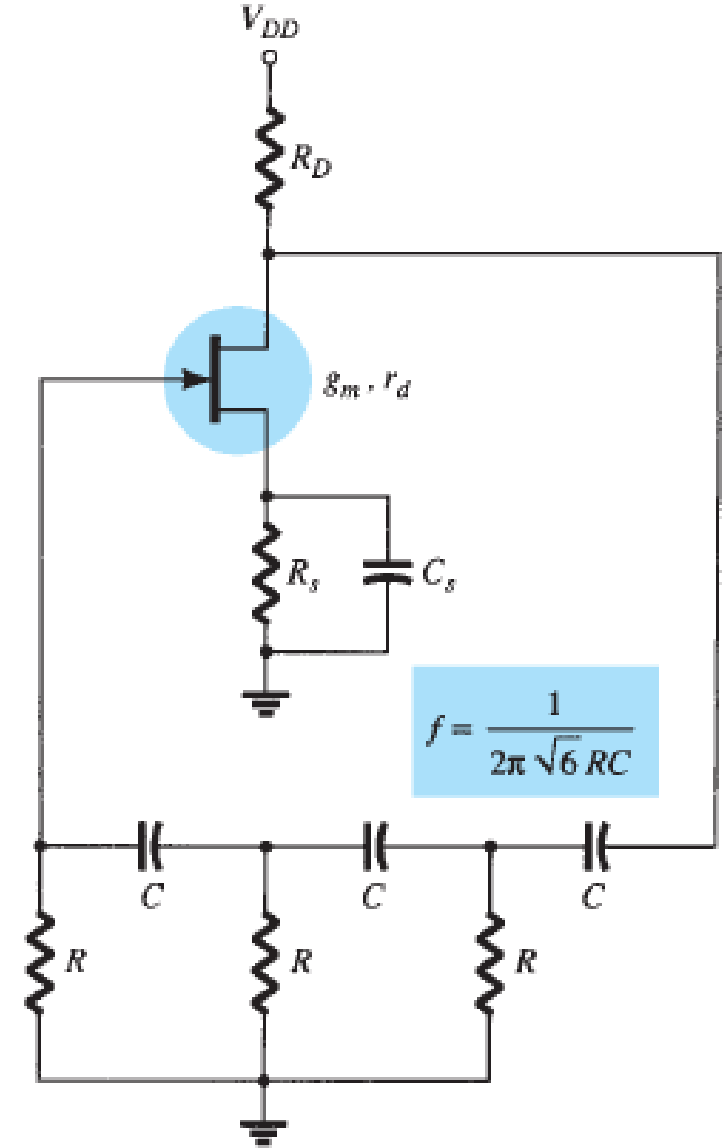

# FET Phase-Shift Oscillator

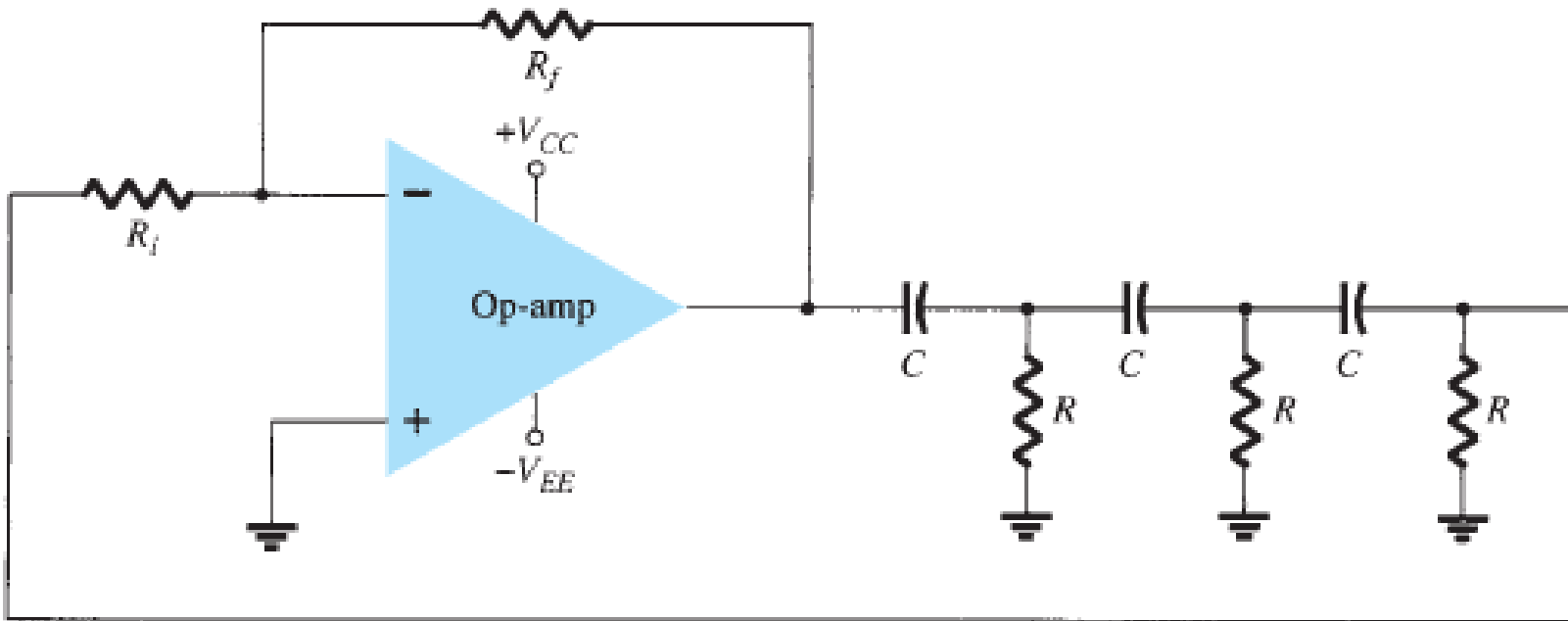


- The output of the op-amp is fed to a three-stage  $RC$  network, which provides the needed  $180^\circ$  of phase shift (at an attenuation factor of  $1/29$ )
- If the op-amp provides gain (set by resistors  $R_i$  and  $R_f$ ) of greater than 29, a loop gain greater than unity results and the circuit acts as an oscillator with

$$f = \frac{1}{2\pi RC\sqrt{6}}$$

# FET Phase-Shift Oscillator

A variety of circuits can be built using that shown in the figure by providing tuning in both the input and output sections of the circuit

<i>Oscillator Type</i>	<i>Reactance Element</i>		
	$X_1$	$X_2$	$X_3$
Colpitts oscillator	$C$	$C$	$L$
Hartley oscillator	$L$	$L$	$C$
Tuned input, tuned output	$LC$	$LC$	—

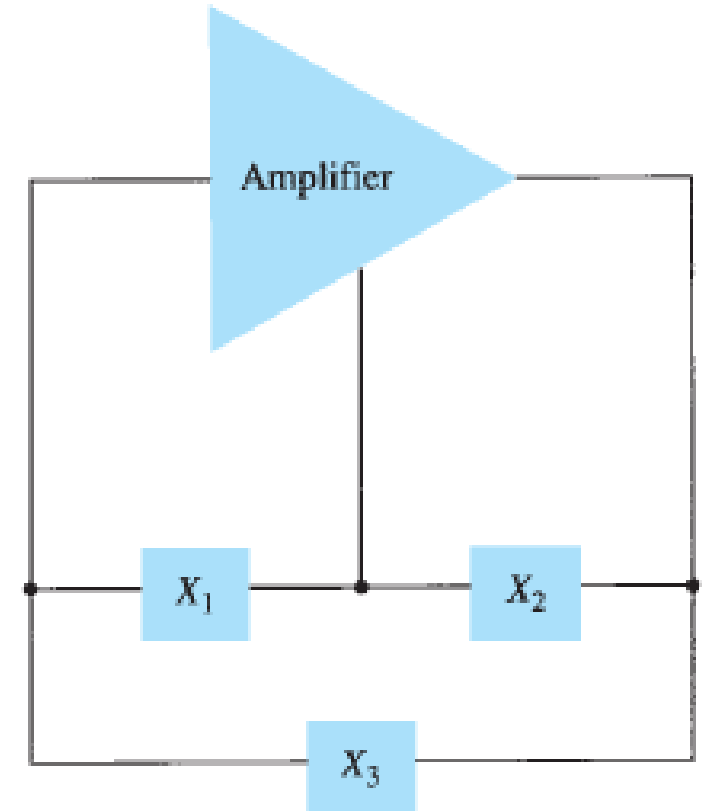



# FET Phase-Shift Oscillator

The oscillator frequency can be found to be

$$f_o = \frac{1}{2\pi LC_{eq}}$$

Where

$$C_{eq} = \frac{C_1 C_2}{C_1 + C_2}$$

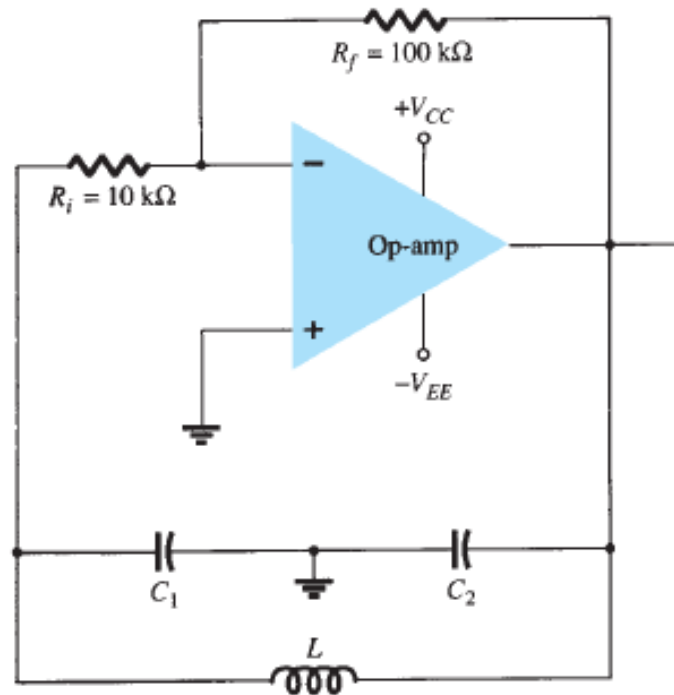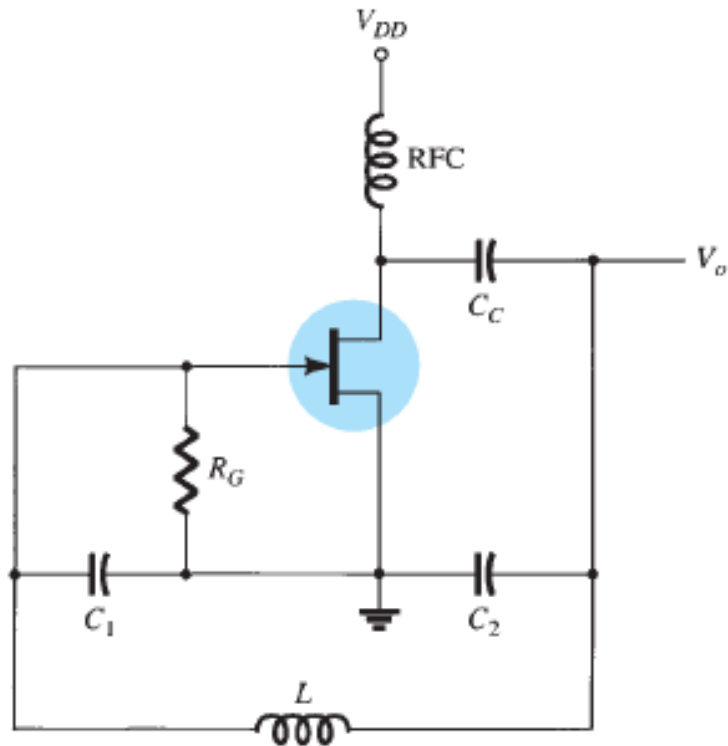

<i>Oscillator Type</i>	<i>Reactance Element</i>		
	$X_1$	$X_2$	$X_3$
Colpitts oscillator	$C$	$C$	$L$
Hartley oscillator	$L$	$L$	$C$
Tuned input, tuned output	$LC$	$LC$	—

# FET Phase-Shift Oscillator

Inductors  $L_1$  and  $L_2$  have a mutual coupling  $M$ , which must be taken into account in determining the equivalent inductance for the resonant tank circuit

The circuit frequency of oscillation is then given approximately by

$$f_o = \frac{1}{2\pi \sqrt{L_{eq}C}}$$

with

$$L_{eq} = L_1 + L_2 + 2M$$

<i>Oscillator Type</i>	<i>Reactance Element</i>		
	$X_1$	$X_2$	$X_3$
Colpitts oscillator	$C$	$C$	$L$
Hartley oscillator	$L$	$L$	$C$
Tuned input, tuned output	$LC$	$LC$	—

